

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**  
**THIRD SEMESTER B.TECH DEGREE EXAMINATION(R&S), DECEMBER 2019**

**Course Code: CS203**

**Course Name: SWITCHING THEORY AND LOGIC DESIGN**

Max. Marks: 100

Duration: 3 Hours

**PART A**

*Answer all questions, each carries 3 marks.*

Marks

- |   |  |     |
|---|--|-----|
| 1 | What is the largest binary number that can be expressed with 16 bits? What are the equivalent decimal and hexadecimal numbers?   | (3) |
| 2 | Perform subtraction on the given unsigned binary numbers using the 2's complement of the subtrahend. Where the result should be negative, find its 2's complement and affix a minus sign.<br>(i) 10011 - 10010                      (ii) 100010 - 100110 | (3) |
| 3 | Find the complement of the following expressions:<br>(i) $xy' + x'y$ (ii) $(a + c)(a + b')(a' + b + c')$   | (3) |
| 4 | State and Prove Absorption law in Boolean Algebra.   | (3) |

**PART B**

*Answer any two full questions, each carries 9 marks.*

- |   |   |            |
|---|---|------------|
| 5 | (a) The value of a float type variable is represented using a single precision 32 bit floating point format IEEE 754 standard that uses 1 bit for the sign, 8 bits for biased exponent and 23 bits for the mantissa. A float type variable X is assigned value of -0.0625. What is the representation of X in hexadecimal notation?<br>(b) Perform the following operations<br>(i) Find the 16's complement of C3DF.<br>(ii) Convert C3DF to binary.<br>(iii) Find the 2's complement of the result in (ii) | (6)<br>(3) |
| 6 | (a) Add and multiply the following numbers without converting them to decimal.<br>(i) Binary numbers 1011 and 101.<br>(ii) Octal numbers 62 and 37<br>(iii) Hexadecimal numbers 2E and 34.<br>(b) Represent the unsigned decimal numbers 791 and 658 in BCD, and then show the steps necessary to form their sum.   | (6)<br>(3) |
| 7 | (a) We can perform logical operations on strings of bits by considering each pair of corresponding bits separately (called bitwise operation). Given two eight-bit strings A = 10110001 and B = 10101100, evaluate the eight-bit result after the following logical operations:<br>(i) AND                      (ii) OR                      (iii) XOR  | (3)        |
|   | (b) Simplify the following Boolean expressions to a minimum number of literals:<br>(i) $x'yz + xz$ (ii) $(x + y)(x + y')$ (iii) $xyz + x'y + xyz'$  | (6)        |

**PART C***Answer all questions, each carries 3 marks.*

- 8 Design a combinational circuit with three inputs and one output. The output of the circuit is 1 when the decimal value of the inputs is less than 3. The output is 0 otherwise. (3)
- 9 Implement the Boolean function  $F(A, B, C, D) = \pi(3, 7, 12)$  with a multiplexer: (3)
- 10 Differentiate between Combinational and Sequential circuits. Give two examples for each. (3)
- 11 Construct a JK flip-flop using a D flip-flop, a two-to-one-line multiplexer, and an inverter. (3)

**PART D***Answer any two full questions, each carries 9 marks.*

- 12 (a) Design a four-bit 2's complementer combinational circuit. The circuit accepts a 4-bit binary number as input and generates the 2's complement of the input. Show that the circuit can be constructed with exclusive-OR gates. (7)
- (b) Predict what the output functions are for a five-bit 2's complementer? (2)
- 13 (a) Show that the characteristic equation for the complement output of a JK flip-flop is:  $Q'(t+1) = J'Q' + KQ$  (3)
- (b) Draw the logic diagram of a 4x16 decoder constructed with two 3x8 decoders (4)
- (c) Implement T flip-flop using NAND gates. (2)
- 14 A sequential circuit has two JK flip-flops A and B and one input x. The circuit is described by the following flip-flop input equations: (9)
- $$J_A = x \quad K_A = B' \quad J_B = x \quad K_B = A$$
- (i) Tabulate the state table.
- (ii) Draw the state diagram of the circuit.
- (iii) Derive the state equations for A(t+1) and B(t+1)

**PART E***Answer any four full questions, each carries 10 marks.*

- 15 (a) Draw and explain the different types of shift registers. (6)
- (b) Explain how shift registers can be used for serial transfer. (4)
- 16 Design and construct a Johnson counter with 8 distinguishable states. Give its timing diagram. (10)
- 17 (a) Design a synchronous counter with the following repeated binary sequence 000, 100, 111, 010, 011 using T Flip Flops. (6)
- (b) Write a note on error detection and correction. (4)
- 18 Find the minimum size of PLA required to implement the following functions? (10)
- $$F(X, Y, Z) = \sum m(1, 3, 5, 7), \quad G(X, Y, Z) = \sum m(0, 2, 4, 6)$$
- 19 (a) Design a BCD ripple counter using T flipflops (6)
- (b) Explain the implementation of full adder using Hardware Description Language (HDL). (4)
- 20 Draw and explain the flow chart for addition and subtraction of two binary numbers in sign magnitude form. (10)